

ISLAMIC UNIVERSITY OF TECHNOLOGY (IUT)
ORGANISATION OF ISLAMIC COOPERATION (OIC)
DEPARTMENT OF ELECTRICAL & ELECTRONIC ENGINEERING

Semester Final Examination
Course No.: EEE 4203
Course Title: Electronics I

Summer Semester, A.Y. 2017-2018
Time: 3 Hours
Full Marks: 150

There are 8(Eight) questions. Answer **any 6 (Six)** questions. Programmable calculators are not allowed. Figures in the margin indicate marks of the part questions. Do not write on this question paper. Assume reasonable value for any missing data.

- 1(a) Find V_o and I for the circuit shown in the Fig. 1(a). v_i is a 1 kHz, 10 V peak sine wave, [09]
sketch the wave form resulting at v_o . What are its positive and negative peak values?
Diodes are ideal.

 


Fig. 1(a)

- (b) For the circuit of Fig. 1(b), a string of three diodes are used to provide a constant voltage [10]
of about 2.1 V. Calculate percentage of change in this regulated voltage caused by
(i) $\pm 10\%$ change in power-supply
(ii) connection of $R_L = 500\ \Omega$ load resistance. Assume $n = 2$.

 


Fig. 1(b)

- (c) Draw the circuit diagram of an AND gate using ideal diodes and describe how AND logic operation is performed in the circuit. [06]

- 2.(a) Find the output wave-shapes for the following (Fig. 2(a)) clippers (diodes are ideal):

 


Fig. 2(a)

- (b) Find the output wave-shapes for the following clippers (diodes are ideal) in Fig. 2(b): [13]

 


Fig. 2(b)

- 3.(a) Using the fact that a silicon diode has $I_S = 10^{-14}$ A at 25 °C and I_S increases by 15% per °C rise in temperature, find the value of I_S at 125 °C. [5]
- (b) Using the diode equation in forward biasing region, find the expression of small signal resistance of a diode. What is the significance of this resistance if the diode is used as a voltage regulator? [10]
- (c) Determine the range of R_L and I_L that will result in load voltage being maintained at 10 V (assume $r_Z = 0$) for the following circuit shown in Fig. 3 (c) [10]

 


Fig. 3(c)

- 4.(a) Explain why a BJT is known as bipolar device. Define β and α of a BJT and establish the relation between them. If the value of α in a BJT is close to unity, what should be the value of the base current? [8]
- (b) Calculate the value of R_1 and R_C for the circuit in Fig. 4(b). The collector current $I_C = 1$ mA and the collector to emitter voltage $V_{CE} = 6$ V. Neglect the base current. [8]

 


Fig. 4(b)

- (c) For the circuit in the Fig. 4(c), it is required to determine the value of the voltage V_{BB} [9]
that results in the transistor operating
(i) in the active mode with $V_{CE} = 5$ V,
(ii) at the edge of saturation,
(iii) deep in saturation with $\beta_{forced} = 10$.
For simplicity, assume that V_{BE} remains constant at 0.7 V. The transistor β is specified to be 50.

 


Fig. 4(c)

- 5.(a) The transistor in the circuit in Fig. 5(a) is specified to have β in the range of 50 to 150. Find the value of R_B that results in saturation with an ODF at least 10. [08]

 


Fig. 5(a)

- b) For the circuit in Fig. 5(b) determine whether the BJT is in active or saturation mode. [12]
Then determine V_E , V_C , V_B , I_E , I_C and I_B .

 


Fig. 5(b)

- c) What is the significance of Q point in a BJT amplifier? Does its location affect the performance of the amplifier? [05]
- 6.(a) Draw a common emitter amplifier circuit. Draw its small signal equivalent circuit and find the expressions of (i) R_{in} (ii) A_v (iii) G_v (iv) A_{us} and (v) R_{O} . [15]
- (b) For the above amplifier of Q. 6(a), $R_B = 100\text{ k}\Omega$, $R_C = 8\text{ k}\Omega$, $R_L = 5\text{ k}\Omega$, $g_m = 40\text{ mA/V}$, $r_\pi = 2.5\text{ k}\Omega$, $r_o = 100\text{ k}\Omega$, $r_e = 25\text{ }\Omega$. If $R_{sig} = 5\text{ k}\Omega$ and the sine-wave v_s is limited to 5 mV peak, what is the maximum allowed peak of v_{sig} and the corresponding peak amplitude of v_o . [10]
- 7.(a) Describe the differences between BJTs and FETs. Why JFETs are widely used in digital ICs? [05]
- (b) Describe the operation principle of a depletion type n-channel JFETs with proper diagrams including semiconductor structure and output characteristics. How can a JFET be used as a variable resistor? [10]
Given $I_{DSS} = 6\text{ mA}$ and $V_P = -4.5\text{ V}$; Using Shockley's equation draw the transfer characteristics of a depletion type n-channel MOSFET. If V_{GS} is positive which region it will operate? What precaution has to be taken to have a positive gate to source voltage? [10]

8.(a) A depletion n-channel MOSFET amplifier has been biased with a configuration of a voltage divider configuration. Draw the circuit diagram for this arrangement. In the voltage divider branch set $R_1 = 110 \text{ M}\Omega$, $R_2 = 10 \text{ M}\Omega$. The drain resistance, $R_D = 1.8 \text{ k}\Omega$ and source resistance $R_S = 750 \Omega$. If $I_{DSS} = 6 \text{ mA}$ and $V_P = -3 \text{ V}$, determine I_{DQ} , V_{GSQ} and V_{DS} . [12]

(b) The fixed bias configuration of a JFET has an operating point defined by $V_{GSQ} = -2 \text{ V}$ [13] and $I_{DQ} = 5.625 \text{ mA}$, with $I_{DSS} = 10 \text{ mA}$ and $V_P = -8 \text{ V}$. The network is shown in Fig. 8(b) with an applied signal V_i . The value of y_{os} is provided as $40 \mu\text{S}$.

- Determine g_m .
- Find r_d .
- Determine Z_i .
- Calculate Z_o .
- Determine the voltage gain A_v .
- Determine A_v ignoring the effects of r_d .

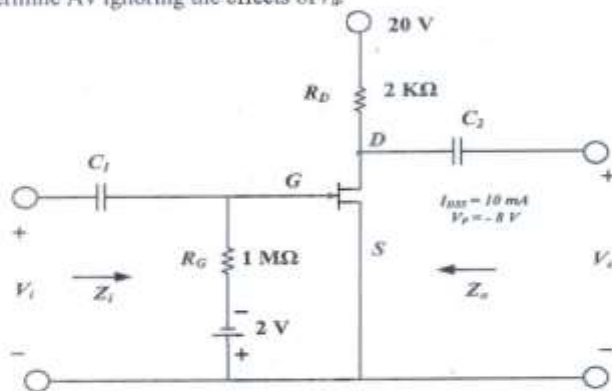


Fig. 8(b)

ISLAMIC UNIVERSITY OF TECHNOLOGY (IUT)
ORGANISATION OF ISLAMIC COOPERATION (OIC)

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

Semester Final Examination
Course No.: EEE 4203
Course Title: Electronics I

Summer Semester, A.Y. 2018-2019
Time: 3 hours
Full Marks: 150

There are 8 (eight) questions. Answer any 6 (six) questions. All questions carry equal marks. Marks in the margin indicate full marks. Programmable calculators are not allowed. Do not write on this question paper. Symbols preserve their usual meaning.

1. a) The input voltage V_i in Fig. 1(a) is a 1 kHz, 20 V peak to peak sine wave. Sketch the resulting output waveform at V_o as indicated. 7

 


Fig. 1(a)

 


Fig. 1(b)

- b) For the above circuit in Fig. 1(b), a string of three diodes are used to provide a constant voltage of about 2.1 volt. Calculate percentage of change in this regulated voltage caused by
(i) $\pm 10\%$ change in power supply.
(ii) Connection of load resistance, R_L . Assume, $n = 2$. 8
- c) Determine the range of values of R_L and I_L for the figure shown in Fig. 1(c). 10

 


Fig. 1(c)

 


Fig. 2(a)

2. a) Find the output waveshape for the clipper shown in Fig. 2(a). Assume, all diodes are ideal 10

- b) Find the output voltage waveshapes for the following clampers (with Si diodes) shown in Fig. 2(b). 15

 


Fig. 2(b)

3. a) What is an Early effect of a BJT? Derive the expression of output resistance considering the Early effect. 8
- b) For the circuit in Fig. 3(b), determine the value of the voltage V_{BB} that results in the transistor 10
operating (i) in the active mode with $V_{CE} = 5$ V, (ii) at the edge of saturation and (iii) deep in
saturation with $\beta_{forced} = 10$. Assume, $V_{BE} = 0.7$ V and $\beta = 50$.

 


Fig. 3(b)

 


Fig. 3(c)

- c) For the circuit shown in Fig. 3(c), calculate the base current, collector current and the collector 7
voltage where $V_{CC} = +5$ V, $V_i = +5$ V, $R_B = R_C = 1$ kΩ and $\beta = 100$. If the transistor is saturated, find
 β_{forced} . What value should R_B be raised to bring the transistor to the edge of saturation?
4. a) For the network of Fig. 4(a), Find I_C , I_B , I_E , V_C and V_E . 10

 


Fig. 4(a)

 


Fig. 4(b)

- b) Analyze the circuit of Fig. 4(b) and find all the node voltages and branch currents. The minimum value of β is specified to be 30. 15

5. a) For the circuit of Fig. 5(a), determine the voltages at all nodes and currents through all branches. Assume, $\beta = 100$. 12

 


Fig. 5(a)

 


Fig. 5(b)

- b) Evaluate the voltages at all nodes and the currents through all branches in the circuit of Fig. 5(b). Assume, $\beta = 100$. 13
6. a) Derive the expression of g_m , r_x and r_e for the small signal model of a BJT. 7
- b) Analyze the transistor amplifier shown in Fig. 6(b) to determine its voltage gain v_o/v_i . Assume, $\beta = 100$ and neglect the early effect. 8

 


Fig. 6 (b)

- c) A CE amplifier utilizes a BJT with $\beta = 100$ is biased at $I_C = 1$ mA and has a collector resistance $R_C = 5$ kΩ. Find R_{in} , R_o and A_{vo} . If amplifier is fed with a signal source having a resistance of 5 kΩ and load resistance $R_L = 5$ kΩ is connected to the output terminal, find the resulting A_v and G_v . 10
7. a) What is the basic difference between JFET and BJT? Write down the advantages and disadvantages of JFET. 5

- b) Determine (i) V_{GSQ} (ii) I_{DQ} (iii) V_{DS} (iv) V_S (v) V_G (vi) V_D for the circuit shown in Fig. 7(b).

10

 


Fig. 7(b)

 


Fig. 7(c)

- c) Determine (i) I_{DQ} and V_{DSQ} (ii) V_D (iii) V_S (iv) V_{GS} (v) V_{DG} for the network of Fig. 7(c). 10
8. a) What is the difference between depletion type MOSFET and enhancement type MOSFET with respect to transfer characteristics? 7
- b) Determine I_{DQ} and V_{DSQ} for the enhancement type MOSFET shown in Fig. 8(b). 8

 


Fig. 8(b)

 


Fig. 8(c)

- c) For the network of Fig. 8(c) $V_{GSQ} = 0.35$ V, $I_{DQ} = 7.6$ mA, $I_{DSS} = 6$ mA, $V_P = -3$ V and $g_{m0} = 10$ μS. 10
- Determine g_m and compare to g_{m0}
 - Find r_d
 - Sketch the ac equivalent network
 - Find Z_i
 - Calculate Z_o
 - Find A_v


Q.1. (a) (i) The model of npn BJT in saturation mode reveals the following equation: 12.5

$$i_C = I_S e^{v_{BE}/V_T} - I_{SC} e^{v_{BC}/V_T}$$


Draw the the i_C vs v_{CE} characteristic of the npn transistor fed with constant emitter current I_E following the above equation. Clearly define different region of operations.

(ii) Find the value of Collector to Emitter voltage at the edge of saturation.

 (iii) For the following figure, find the value of the voltage V_{BB} in the transistor operating in deep saturation with $\beta_{forced}=8$




 1.(b) For the circuit in the following Figure, find the highest voltage to which the base can be raised while the transistor remains in the active mode. Assume $\alpha = 1$. 12.5




Question Number 2

 
- Q.2 (a) Determine the voltages at all nodes and the currents through all branches. 12.5
The minimum value of β is specified to be 20.



 - 2.(b) Evaluate the voltages at all nodes and the currents through all branches in the circuit of the following circuit by replacing the feeding voltage to the bases $+5\text{ V}$ by -5 V . Assume $\beta = 100$ if transistor operates in active region. 12.5




 3. (a) In the circuit of the following figure, V_{BE} is adjusted to yield a dc collector current of 1 mA. Let $V_{CC} = 15$ V, $R_C = 10$ k Ω , and $\beta = 100$. Find the voltage gain If $v_{be} = 0.005 \sin \omega t$ volt, find $v_{c(t)}$ and $i_b(t)$. 12.5




- (b) Consider a CB amplifier utilizing a BJT biased at $I_C = 1$ mA and with $R_C = 5$ k Ω . Determine R_{in} , A_{vo} , R_o , if the amplifier is loaded in $R_L = 5$ k Ω , what value of A_v results? What G_v is obtained if $R_{sig} = 5$ k Ω ? 12.5

 - Q.4. (a) (i) What are the main advantages of FETs over BJTs? 04
(ii) Using the following figure, sketch the transfer characteristics directly from the drain characteristics. Using the following figure to establish the values of I_{DSS} and V_p , sketch the transfer characteristics using Shockley's equation 8.5



 4. (b) For the self-bias configuration of the following figure, determine: (i) I_{DQ} and V_{DSQ} . (ii) V_{GS} and V_D . 12.5



OR

- (b) Determine Z_i , Z_o , and A_v for the following network.

