

ISLAMIC UNIVERSITY OF TECHNOLOGY (IUT)  
ORGANISATION OF ISLAMIC COOPERATION (OIC)

DEPARTMENT OF COMPUTER SCIENCE AND ENGINEERING

Mid-Semester Examination

Course No.: Phy 4241

Course Title: Physics II

Summer Semester, A. Y. 2017-2018

Time: 90 Minutes

Full Marks: 75

There are 4 (four) questions. Answer any 3 (three) questions. All questions carry equal marks. Marks in the margin indicate full marks. Programmable calculators are not allowed. Do not write on this question paper. All symbols bear their usual meanings.

1. a) For the circuit shown in Fig. 1(a), find  $V_0 / V_s$  in terms of  $\alpha$ ,  $R_1$ ,  $R_2$ ,  $R_3$ , and  $R_4$ . 08  
If  $R_1 = R_2 = R_3 = R_4$ , what value of  $\alpha$  will produce  $|V_0 / V_s| = 15$ ?

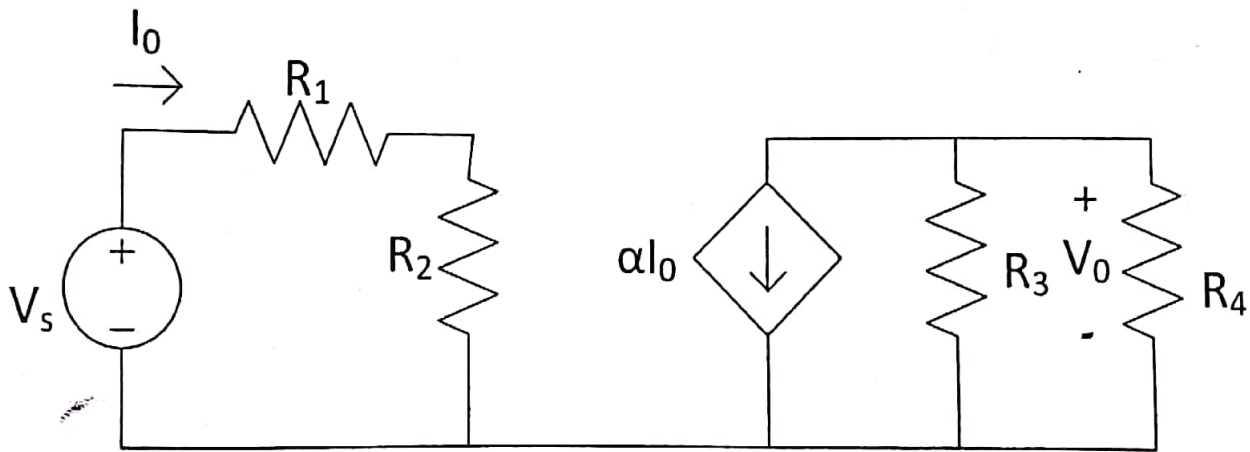


Fig. 1(a)

- b) Obtain the equivalent resistance,  $R_{ab}$  in the circuit of Fig. 1(b). All the resistors have a value of  $40 \Omega$ . 13

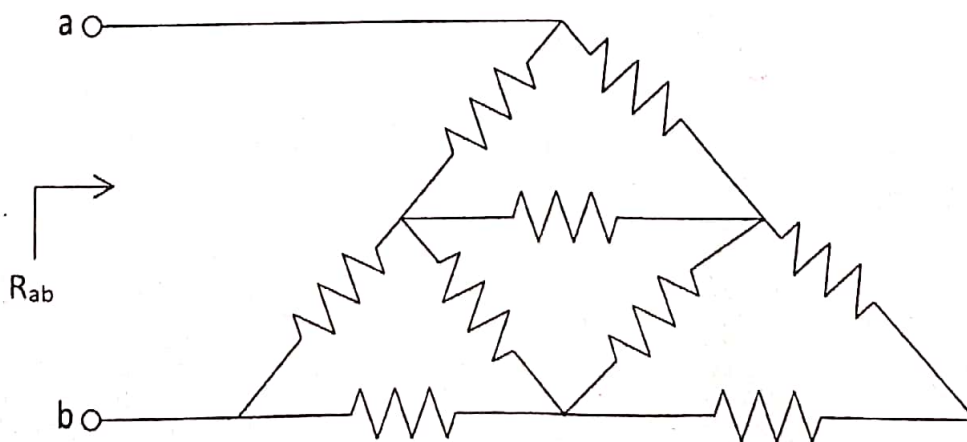


Fig. 1(b)

- c) Define supermesh and supernode.

2. a) Find the node voltages of the circuit shown in Fig. 2(a).

15

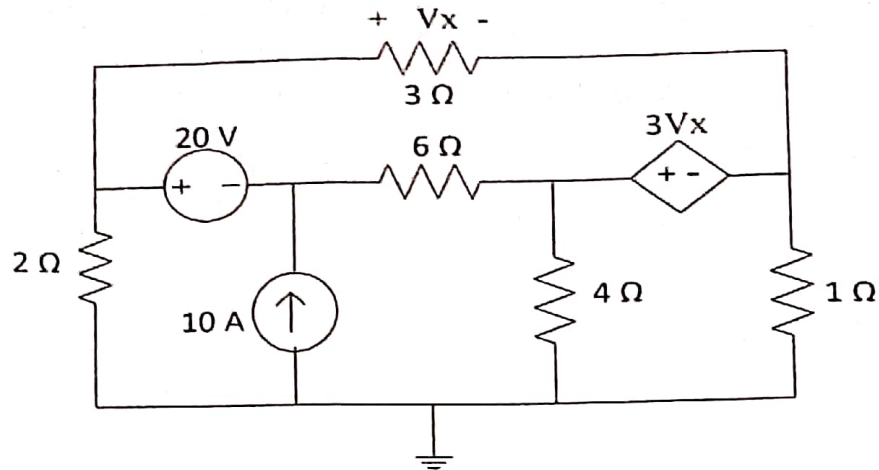


Fig. 2(a)

- b) Write one use of  $\Delta$ -Y transformation. Find the current delivered by the source in the circuit shown in Fig. 2(b).

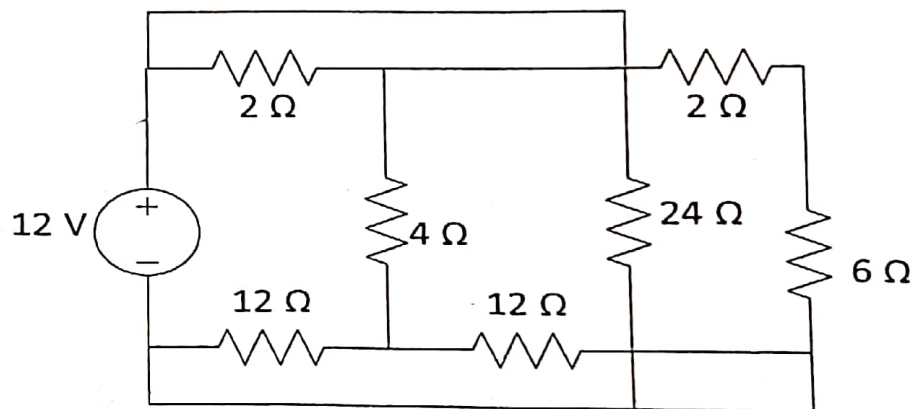


Fig. 2(b)

3. a) Use both resistance and source combinations, as well as, current division, in the circuit of Fig. 3(a) to find the power absorbed by the 1  $\Omega$  resistor.

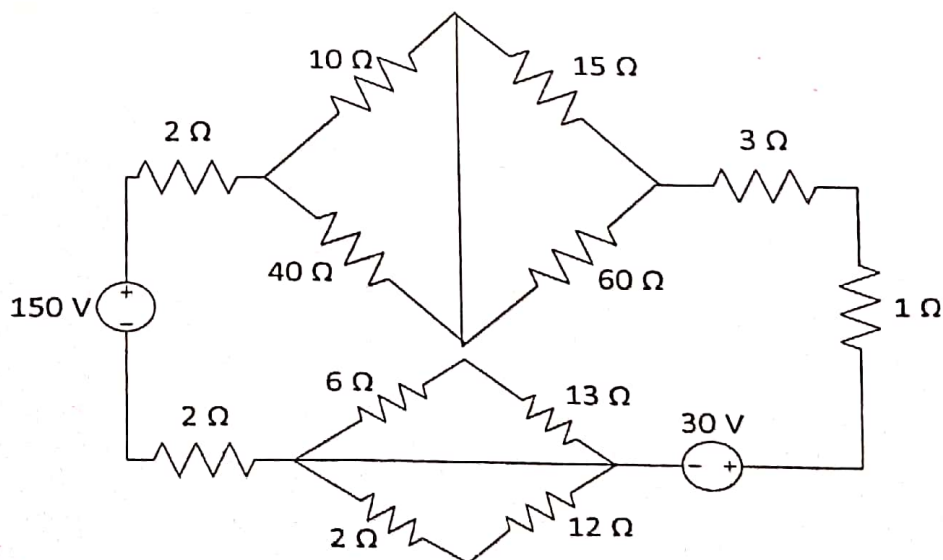


Fig. 3(a)

- b) Find the values of  $R_1$  and  $R_2$  in the circuit of Fig. 3(b) if the voltmeter and ammeter read 6 V and 0.6 A, respectively. 10

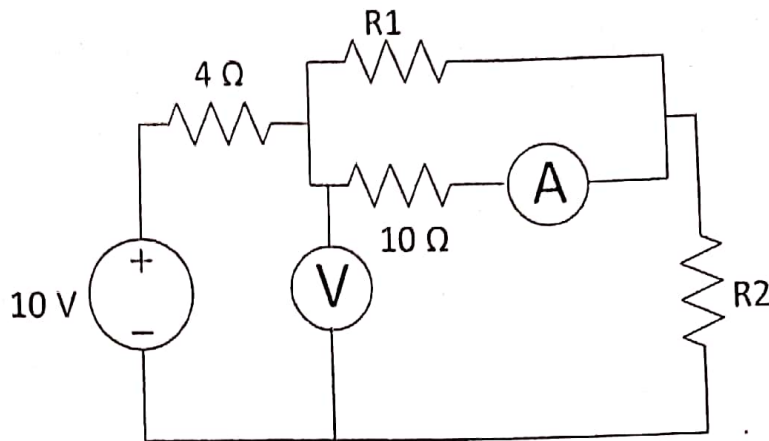


Fig. 3(b)

4. a) In the circuit shown in Fig. 4(a), find the terminal voltage,  $V_{ab}$  using superposition theorem. 12

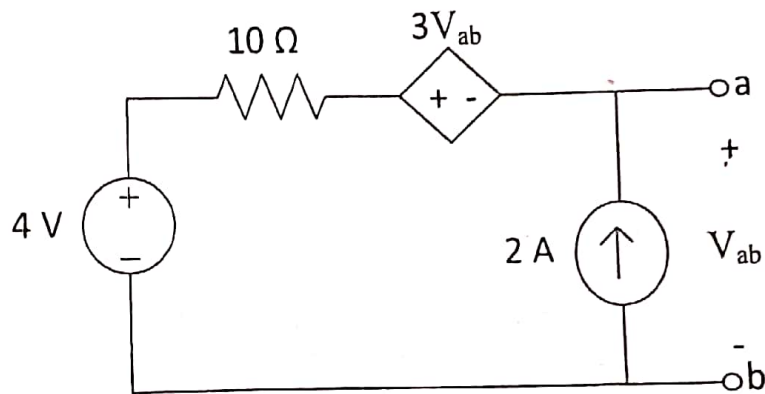


Fig. 4(a)

- b) The variable resistor in the circuit shown in Fig. 4(b) is adjusted for maximum power transfer to  $R_L$ . Find the value of  $R_L$ . Also find the maximum power that can be delivered to  $R_L$ . 13

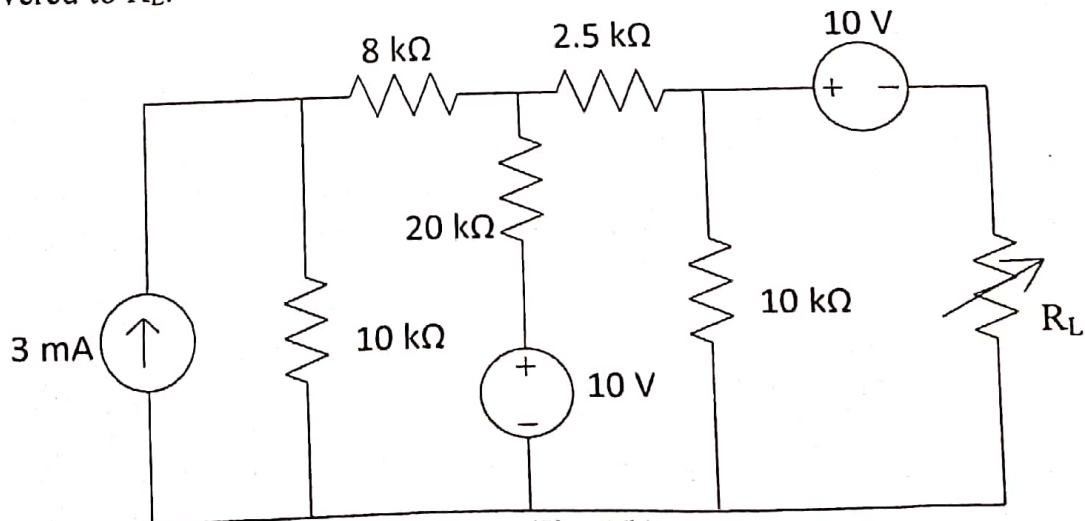


Fig. 4(b)

ISLAMIC UNIVERSITY OF TECHNOLOGY (IUT)  
ORGANISATION OF ISLAMIC COOPERATION (OIC)

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

Mid-Semester Examination  
Course No.: Phy 4241  
Course Title: Physics II

Summer Semester, A.Y. 2016-2017  
Time: 90 Minutes  
Full Marks: 75

There are 4 (four) questions. Answer any 3 (three) questions. All questions carry equal marks. Marks in the margin indicate full marks. Programmable calculators are not allowed. Do not write on this question paper.

1. a) Find the equivalent conductance for "s" number of resistors connected in parallel. 5
- b) Find  $V_1$  and  $V_2$  in the Fig. 1(b) using nodal analysis. 10

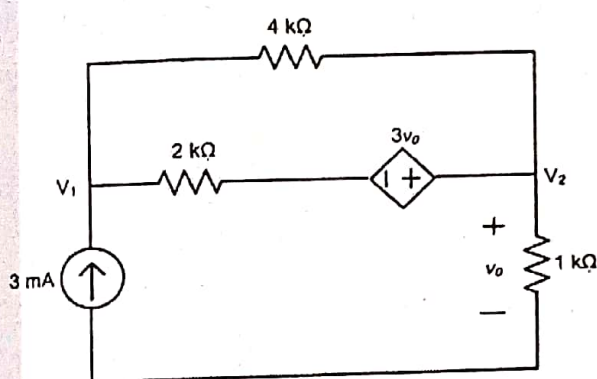


Fig. 1(b)

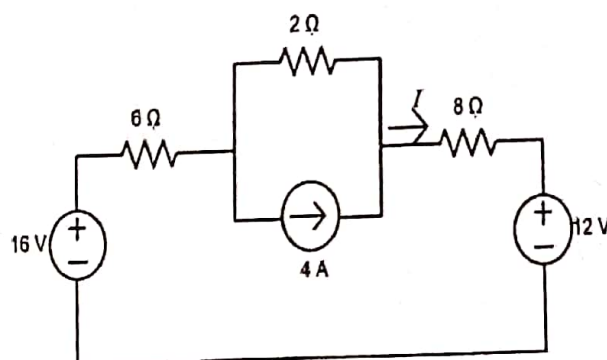


Fig. 1(c)

- c) By superposition principle find  $I$  in the circuit shown in Fig. 1(c). 10
2. a) Prove that each resistor in the  $Y$  network is the product of the resistors in the two adjacent  $\Delta$  branches, divided by the sum of the three  $\Delta$  resistors. 5
- b) Find  $V_o$  and  $I_o$  in the following circuit shown in Fig. 2(b). 10

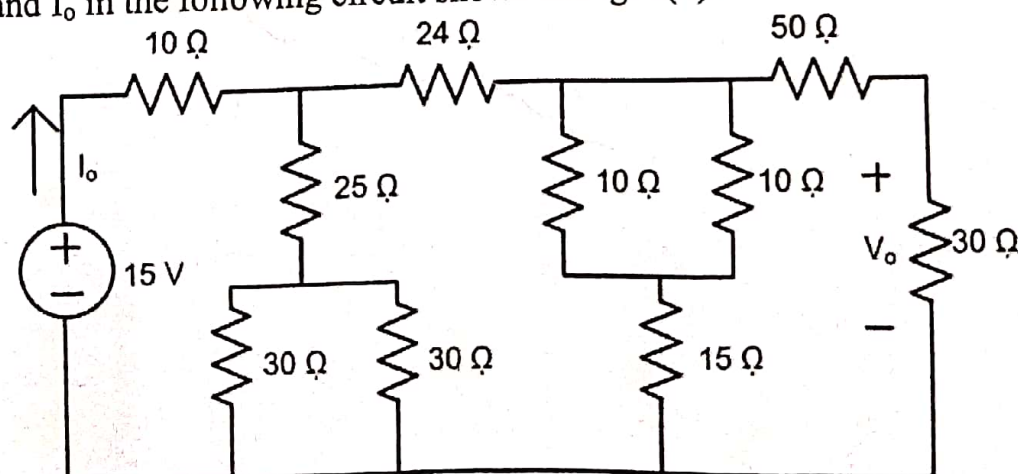


Fig. 2(b)



c) Find the Thevenin equivalent at terminals a-b in the Fig. 2(c).

10

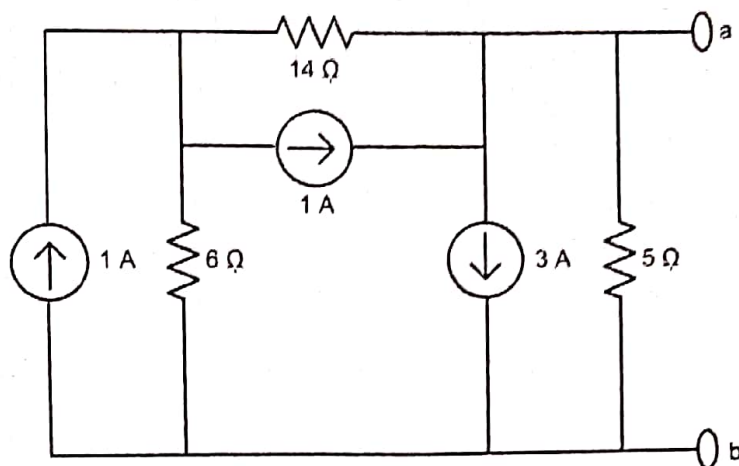


Fig. 2(c)

3. a) Prove that maximum power transfer occurs when  $R_L$  is equal to  $R_{TH}$  and find the expression of  $P_{max}$  for maximum power transfer.

5

b) In the circuit shown in Fig. 3(b) find  $R_{eq}$  and  $I_o$ .

10

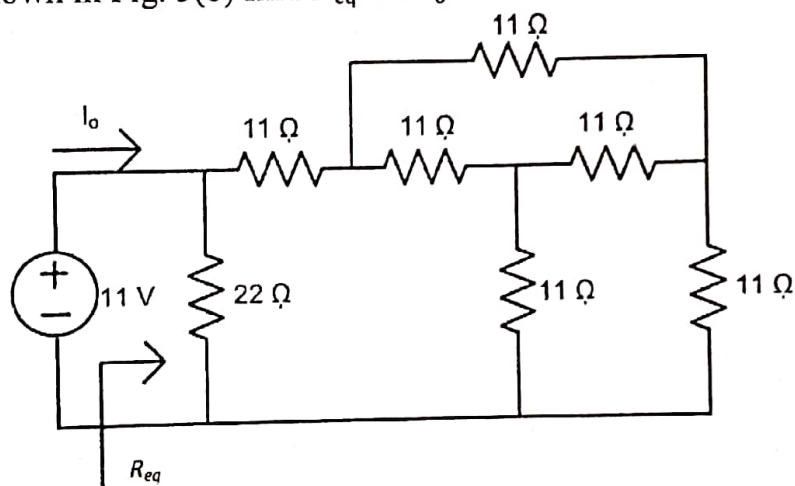


Fig. 3(b)

c) For the following circuit shown in Fig. 3(c) find  $I_1$  to  $I_4$  using mesh analysis.

10

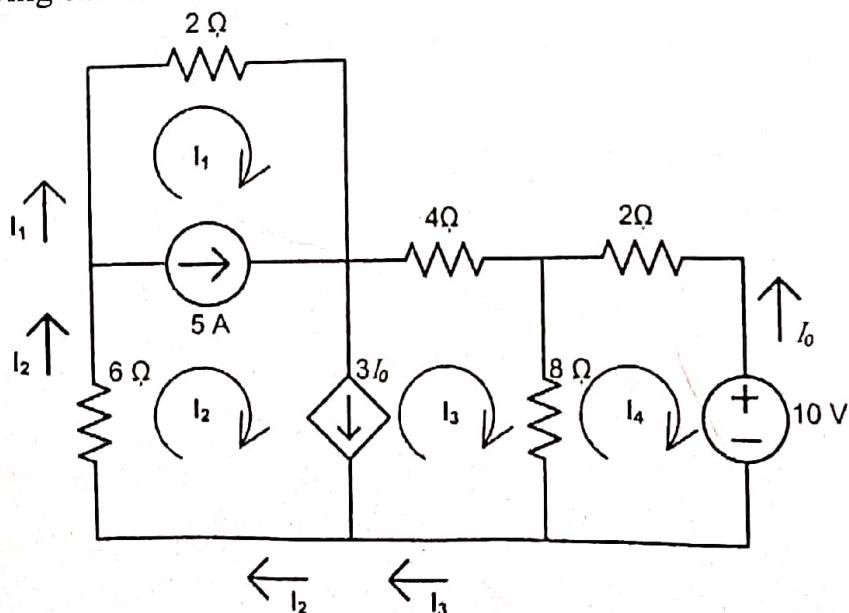


Fig. 3(c)

4. a) Find the phase angle between  $i_1 = -4 \sin(377t + 25^\circ)$  and  $i_2 = 5 \cos(377t - 40^\circ)$ . State which sinusoid is leading. Show them graphically.
- b) Find  $v(t)$  and  $i(t)$  in the following circuit shown in Fig. 4(b).

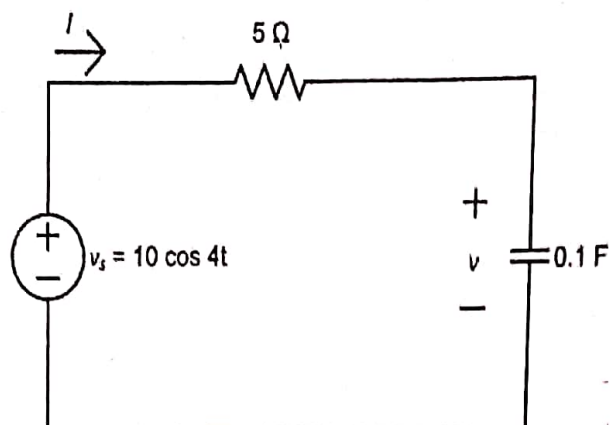


Fig. 4(b)

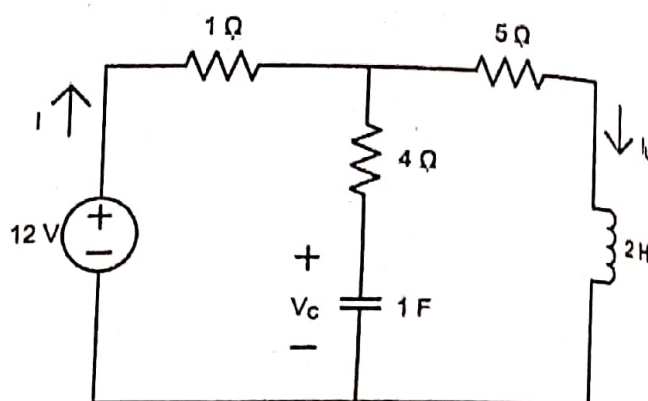


Fig 4(c)

- c) Determine  $I$ ,  $V_C$ ,  $I_L$  and the energy stored in the capacitor and inductor in the circuit shown in Fig. 4(c).

ISLAMIC UNIVERSITY OF TECHNOLOGY (IUT)  
ORGANISATION OF ISLAMIC COOPERATION (OIC)

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

Mid-Semester Examination  
Course No.: Phy 4241  
Course Title: Physics II

Summer Semester, A.Y. 2015-2016  
Time: 90 Minutes  
Full Marks: 75

There are 4 (four) questions. Answer any 3 (three) questions. All questions carry equal marks. Marks in the margin indicate full marks. Programmable calculators are not allowed. Do not write on this question paper.

1. a) Find the equivalent resistance with respect to terminals A and B in the circuit of Fig. 1(a). Assume all the resistance values are equal to 1 k $\Omega$ . 15

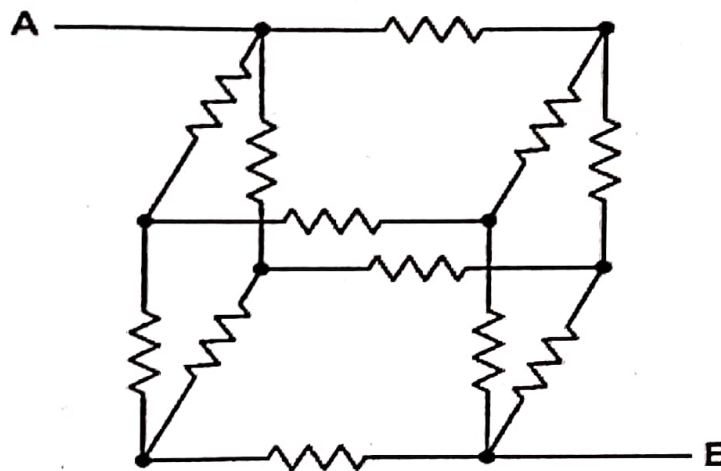


Fig. 1(a)

- b) Assume a current of 3 ampere is entering through the terminal A in the circuit of Fig. 1(a). Now determine all the branch currents and show them in a diagram. 10
2. a) Calculate the value of  $I_1$  from the circuit in Fig. 2(a). 15

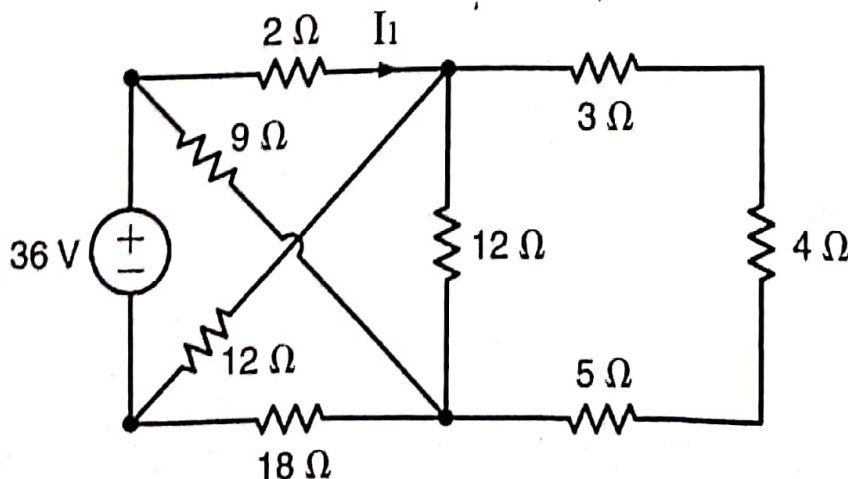


Fig. 2(a)

- b) State the maximum power transfer theorem. For a circuit with ideal source, derive the condition for maximum power transfer with power vs. load graph. 10

3. a) Use mesh analysis to obtain  $i_o$  in the circuit of Fig. 3(a).

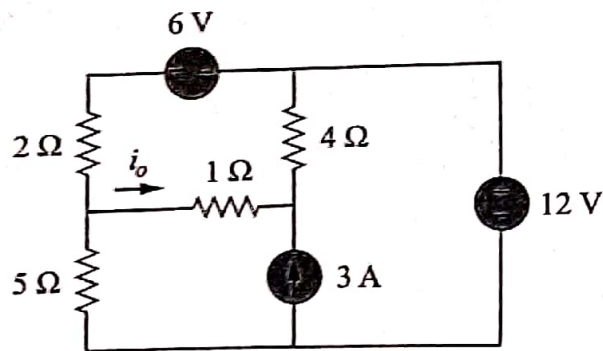


Fig. 3(a)

- b) Derive the equations to convert a delta connected resistance network to an equivalent wye connected resistance network and vice-versa.

4. a) Find out all the node voltages in the circuit of Fig. 4(a).

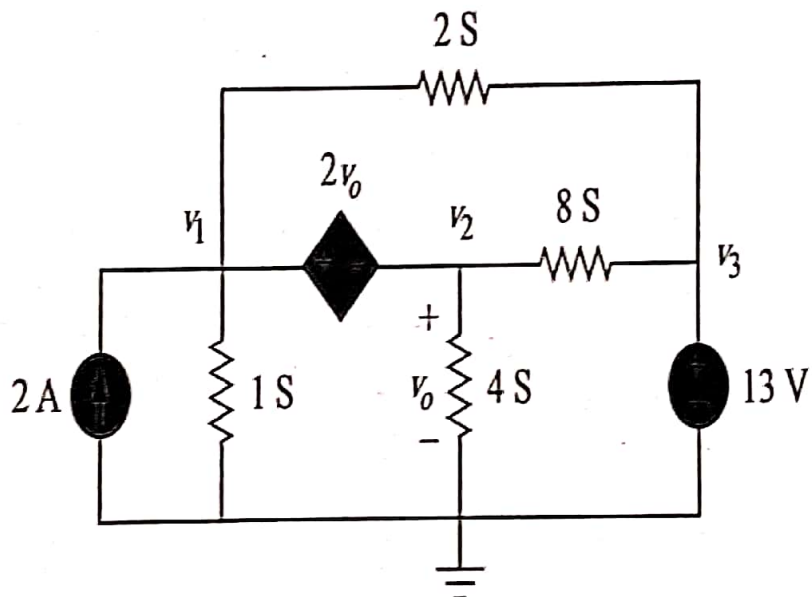


Fig. 4(a)

- b) Determine the value of  $R_L$  when maximum power is transferred in  $R_L$  in the circuit of Fig. 4(b). What is the maximum power?

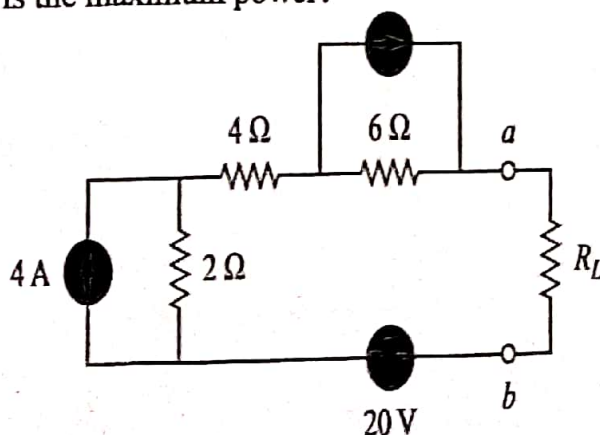


Fig. 4(b)